



Birla Vishvakarma Mahavidyalaya
Engineering Collage (An Autonomous Institution)
Vallabh Vidyanagar - 388 120
Affiliated to Gujarat Technological University

A.Y. 2023

Assignment : II

Course Title: Digital System Design

Name: Galaiya Tushar Jagdishbhai

Id no: 21EL054

Batch: C04

Course Code: 3EL42


Q-1 Design 4-bit Ripple Carry Adder with the help of 1-bit adder.

CODE :

```
1  module full_adder(  
2      input a,  
3      input b,  
4      input Cin,  
5      output sum,  
6      output cout  
7  );  
8  
9      assign sum = a ^ b ^ Cin;  
10     assign cout = (a * b) | (b * Cin) | (a * Cin);  
11  
12 endmodule  
13  
14 module ripple_carry(  
15     input [3:0] a,  
16     input [3:0] b,  
17     input cin,  
18     output [3:0] s,  
19     output cout  
20 );  
21  
22     wire c1,c2,c3;  
23  
24     full_adder fa1(a[0],b[0],cin,s[0],c1);  
25     full_adder fa2(a[1],b[1],c1,s[1],c2);  
26     full_adder fa3(a[2],b[2],c2,s[2],c3);  
27     full_adder fa4(a[3],b[3],c3,s[3],cout);  
28  
29 endmodule
```

TESTBENCH :

```
1  module ripple_carry_tb;
2
3      reg [3:0] a;
4      reg [3:0] b;
5      reg cin;
6      wire [3:0] s;
7      wire cout;
8
9      initial begin
10
11          $monitor("a = %b | b = %b | cin = %b | s = %b | cout = %b",a,b,cin,s,cout);
12
13      end
14
15      ripple_carry uut(a,b,cin,s,cout);
16
17      initial begin
18
19          #100 a = 4'b0000 ; b = 4'b0000 ; cin = 0;
20          #100 a = 4'b0001 ; b = 4'b0001 ; cin = 0;
21          #100 a = 4'b0011 ; b = 4'b0011 ; cin = 0;
22          #100 a = 4'b0111 ; b = 4'b0111 ; cin = 0;
23          #100 a = 4'b1111 ; b = 4'b1111 ; cin = 0;
24          #100 a = 4'b0000 ; b = 4'b0000 ; cin = 1;
25          #100 a = 4'b0001 ; b = 4'b0001 ; cin = 1;
26          #100 a = 4'b0011 ; b = 4'b0011 ; cin = 1;
27          #100 a = 4'b0111 ; b = 4'b0111 ; cin = 1;
28          #100 a = 4'b1111 ; b = 4'b1111 ; cin = 1;
29          #100 $finish;
30
31      end
32      initial begin
33          $dumpfile("dump.vcd");
34          $dumpvars(0);
35      end
36  endmodule
```

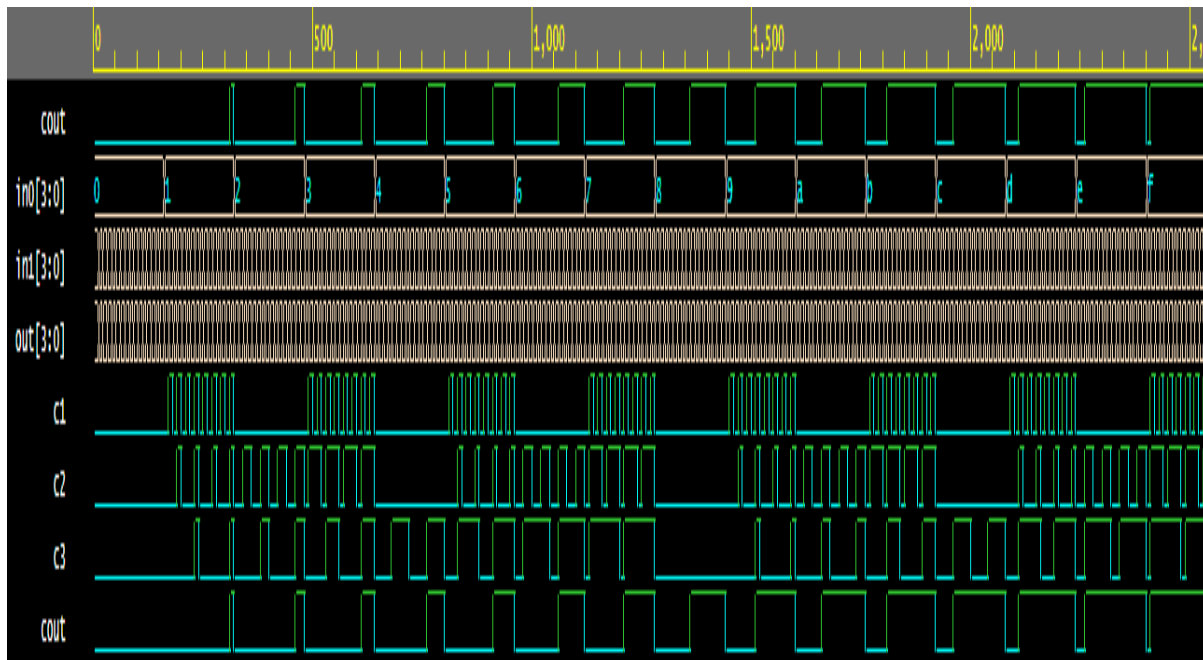OUTPUT :

Q-2 Design D-flipflop and reuse it to implement 4-bit Johnson Counter.

VERILOG CODE :

```
1  module Dff(  
2      input clk,  
3      input reset,  
4      input d,  
5      output reg q  
6  );  
7  
8      always @ (posedge clk)  
9      begin  
10         if(reset)  
11             q=0;  
12  
13         else if(clk)  
14  
15             q = d ;  
16     end  
17 endmodule  
  
1  module _4bit_johnson_counter(  
2      input clk,  
3      input reset,  
4      output [3:0] q  
5  );  
6  
7      Dff d1(clk,reset,~q[3],q[0]);  
8      Dff d2(clk,reset,q[0],q[1]);  
9      Dff d3(clk,reset,q[1],q[2]);  
10     Dff d4(clk,reset,q[2],q[3]);  
11  
12 endmodule
```

TESTBENCH :

```

1    module rbit_johnson_counter_tb;
2
3    reg clk,reset;
4    wire [3:0] q;
5
6    _4bit_johnson_counter uut(clk,reset,q);
7
8    initial
9    begin
10
11        reset = 1'b1;
12        clk = 1'b1;
13
14    end
15
16    always #10 clk = ~clk;
17
18    initial
19    begin
20        #00 reset = 1'b1;
21        #20 reset = 1'b0;
22        #500 $finish;
23
24    end
25
26    endmodule

```

OUTPUT:

```

0 clk=0, out= xxxx, reset=1
5 clk=1, out= 0000, reset=1
10 clk=0, out= 0000, reset=1
15 clk=1, out= 0000, reset=1
20 clk=0, out= 0000, reset=0
25 clk=1, out= 0001, reset=0
30 clk=0, out= 0001, reset=0
35 clk=1, out= 0011, reset=0
40 clk=0, out= 0011, reset=0
45 clk=1, out= 0111, reset=0
50 clk=0, out= 0111, reset=0
55 clk=1, out= 1111, reset=0
60 clk=0, out= 1111, reset=0
65 clk=1, out= 1110, reset=0
70 clk=0, out= 1110, reset=0
75 clk=1, out= 1100, reset=0
80 clk=0, out= 1100, reset=0
85 clk=1, out= 1000, reset=0
90 clk=0, out= 1000, reset=0
95 clk=1, out= 0000, reset=0
100 clk=0, out= 0000, reset=0

```

Q-3 Reuse 2:1 Mux code to implement 8:1 Mux.

VERILOG CODE :

```
1  module mux__21(  
2      input x0,  
3      input x1,  
4      input s,  
5      output out  
6  );  
7  
8      assign out = x0*~s | x1*s;  
9  
10 endmodule  
  
1  module mux_81(  
2      input [7:0] x,  
3      input [2:0] s,  
4      output out  
5  );  
6  
7      wire k1,k2,k3,k4,k5,k6;  
8  
9      mux__21 m1(x[0],x[1],s[0],k1);  
10     mux__21 m2(x[2],x[3],s[0],k2);  
11     mux__21 m3(x[4],x[5],s[0],k3);  
12     mux__21 m4(x[6],x[7],s[0],k4);  
13     mux__21 m5(k1,k2,s[1],k5);  
14     mux__21 m6(k3,k4,s[1],k6);  
15     mux__21 m7(k5,k6,s[2],out);  
16  
17  
18 endmodule
```


TESTBENCH :

```

1  module mux_81_tb;
2
3  reg [7:0]x;
4  reg [2:0]s;
5  wire out;
6
7  initial begin
8
9      $monitor( " %t | x = %b | s2 = %b | s1 = %b | s0 = %b | out = %b " , $time,x,s[2],s[1],s[0],out);
10
11  end
12
13  mux_81 uut(x,s,out);
14
15  initial begin
16      x = 8'b10101010;
17
18      #100 x=8'b10101010; s[2]= 0 ; s[1]= 0 ; s[0]= 0;
19      #100 x=8'b10101010; s[2]= 0 ; s[1]= 0 ; s[0]= 1;
20      #100 x=8'b10101010; s[2]= 0 ; s[1]= 1 ; s[0]= 0;
21      #100 x=8'b10101010; s[2]= 0 ; s[1]= 1 ; s[0]= 1;
22      #100 x=8'b10101010; s[2]= 1 ; s[1]= 0 ; s[0]= 0;
23      #100 x=8'b10101010; s[2]= 1 ; s[1]= 0 ; s[0]= 1;
24      #100 x=8'b10101010; s[2]= 1 ; s[1]= 1 ; s[0]= 0;
25      #100 x=8'b10101010; s[2]= 1 ; s[1]= 1 ; s[0]= 1;
26      #100 $finish;
27
28  end
29  initial begin
30
31      $dumpfile("dump.vcd");
32      $dumpvars(0);
33
34  end
35  endmodule

```

OUTPUT:-

 

Q-4 Design a Full Subtractor with Gate Level Modelling Style (Use primitive gates).

VERILOG CODE :

```
1  module and_21(  
2      input x,  
3      input y,  
4      output z  
5  );  
6  
7      assign z = x*y;  
8  endmodule
```

```
1  module or_21(  
2      input x,  
3      input y,  
4      output z  
5  );  
6  
7      assign z = x|y;  
8  endmodule
```

```
1  module xor_21(  
2      input x,  
3      input y,  
4      output z  
5  );  
6  
7      assign z=x^y;  
8  endmodule
```

```
1  module full_subtractor_gate_level(  
2      input x,  
3      input y,  
4      input z,  
5      output difference,  
6      output borrow  
7  );  
8  
9      xor_21 x1(x,y,k1);  
10     xor_21 x2(k1,z,difference);  
11  
12     and_21 a1(~x,y,k2);  
13     and_21 a2(~x,z,k3);  
14     and_21 a3(y,z,k4);  
15  
16     or_21 o1(k2,k3,k5);  
17     or_21 o2(k5,k4,borrow);  
18  
19 endmodule
```


TESTBENCH :

```

1  module full_subtractor_tb;
2
3  reg x,y,z;
4  wire difference,borrow;
5
6  initial begin
7
8      $monitor($time | "x = %b | y = %b | z = %b | diff = %b | borrow = %b ",x,y,z,difference,borrow);
9
10 end
11
12 full_subtractor_gate_level uut(x,y,z,difference,borrow);
13
14
15 initial begin
16
17     #000 x=0; y=0; z=0;
18     #100 x=0; y=0; z=1;
19     #100 x=0; y=1; z=0;
20     #100 x=0; y=1; z=1;
21     #100 x=1; y=0; z=0;
22     #100 x=1; y=0; z=1;
23     #100 x=1; y=1; z=0;
24     #100 x=1; y=1; z=1;
25
26     #100 $finish;
27
28 end
29
30 initial begin
31
32     $dumpfile("dump.vcd");
33     $dumpvars(0);
34
35 end
36 endmodule

```

OUTPUT :

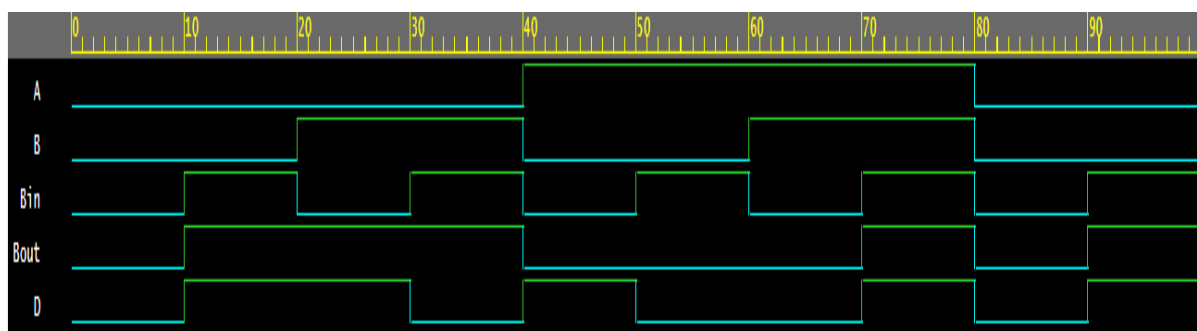

Q-5 Design a 2X4 decoder using gate level modelling.

VERILOG CODE :

```
1      module decoder_24_gate_level(  
2          input x1,  
3          input x2,  
4          output y1,  
5          output y2,  
6          output y3,  
7          output y4  
8      );  
9  
10         and a1(y1,~x1,~x2);  
11         and a2(y2,~x1,x2);  
12         and a3(y3,x1,~x2);  
13         and a4(y4,x1,x2);  
14  
15     endmodule
```

TESTBENCH :

```

1  module decoder_24_tb;
2      reg x1,x2;
3      wire y1,y2,y3,y4;
4
5      initial begin
6
7          $monitor(" %t | x1 = %b | x2 = %b | y1 = %b | y2 = %b | y3 = %b | y4 = %b ",$time,x1,x2,y1,y2,y3,y4);
8
9      end
10     decoder_24_gate_level uut(x1,x2,y1,y2,y3,y4);
11     initial begin
12
13         #000 x1=0; x2=0;
14         #100 x1=0; x2=1;
15         #100 x1=1; x2=0;
16         #100 x1=1; x2=1;
17         #100 $finish;
18
19     end
20
21     initial begin
22
23         $dumpfile("dump.vcd");
24         $dumpvars(0);
25
26     end
27
28 endmodule

```

OUTPUT:-

```

# KERNEL: en=0 a=x b=x y=xxxx
# KERNEL: en=1 a=0 b=0 y=1111
# KERNEL: en=1 a=0 b=1 y=1111
# KERNEL: en=1 a=1 b=0 y=1111
# KERNEL: en=1 a=1 b=1 y=1111

```

Q-6 Design a 4x1 mux using operators. (Use data flow)

VERILOG CODE :

```
1      module mux_41_operator(  
2          input x1,  
3          input x2,  
4          input x3,  
5          input x4,  
6          input s0, s1,  
7          output y  
8      );  
9          assign y = s1 ? ( s0 ? x4:x3) : ( s0 ? x2:x1);  
10     endmodule
```

TESTBENCH :

```
1      module mux_41__tb;
2
3      reg x1,x2,x3,x4,s0,s1;
4      wire y;
5
6      initial begin
7
8          $monitor(" %t | s0 = %b | s1 = %b | y = %b ",$time,s0,s1,y);
9
10     end
11     mux_41__operator uut(x1,x2,x3,x4,s0,s1,y);
12     initial begin
13         x1=1;
14         x2=1;
15         x3=1;
16         x4=1;
17
18         #000 s0=0; s1=0;
19         #100 s0=0; s1=1;
20         #100 s0=1; s1=0;
21         #100 s0=1; s1=1;
22         #100 $finish;
23
24     end
25     initial begin
26
27         $dumpfile("dump.vcd");
28         $dumpvars(0);
29
30     end
31
32     endmodule
```

OUTPUT :

```
sel = 00 -> i3 = 0, i2 = 1 ,i1 = 0, i0 = 1 -> y = 1  
sel = 01 -> i3 = 0, i2 = 1 ,i1 = 0, i0 = 1 -> y = 0  
sel = 11 -> i3 = 0, i2 = 1 ,i1 = 0, i0 = 1 -> y = 0  
sel = 01 -> i3 = 0, i2 = 1 ,i1 = 0, i0 = 1 -> y = 0
```


Q-7 Design a Full adder using half adder.

VERILOG CODE:

```
1  module half_adder(  
2      input x,  
3      input y,  
4      output sum,  
5      output carry  
6  );  
7  
8      assign sum = x^y;  
9      assign carry = x*y;  
10 endmodule  
  
1  module or_21(  
2      input x,  
3      input y,  
4      output z  
5  );  
6      assign z= x|y;  
7  endmodule  
  
1  module fulladder_using_halfadder(  
2      input x,  
3      input y,  
4      input z,  
5      output sum,  
6      output carry  
7  );  
8  
9      half_adder ha1 ( .x(x), .y(y), .sum(k1), .carry(c1));  
10     half_adder ha2 ( .x(k1), .y(z), .sum(sum), .carry(c2));  
11  
12     or_21 o1( .x(c1),.y(c2),.z(carry));  
13 endmodule
```

TESTBENCH :

```

1  module fulladder_using_half_tb;
2
3  reg x,y,z;
4  wire carry,sum;
5
6  initial begin
7
8      $monitor($time | "x = %b | y = %b | z = %b | sum = %b | carry = %b ",x,y,z,carry,sum);
9
10 end
11
12 fulladder_using_halfadder uut(x,y,z,carry,sum);
13
14
15 initial begin
16
17     #000 x=0; y=0; z=0;
18     #100 x=0; y=0; z=1;
19     #100 x=0; y=1; z=0;
20     #100 x=0; y=1; z=1;
21     #100 x=1; y=0; z=0;
22     #100 x=1; y=0; z=1;
23     #100 x=1; y=1; z=0;
24     #100 x=1; y=1; z=1;
25
26     #100 $finish;
27
28 end
29
30 initial begin
31
32     $dumpfile("dump.vcd");
33     $dumpvars(0);
34
35 end
36
37 endmodule

```

OUTPUT :

```

At time 0: a=0 b=0, cin=0, sum=0, carry=0
At time 1: a=0 b=0, cin=1, sum=1, carry=0
At time 2: a=0 b=1, cin=0, sum=1, carry=0
At time 3: a=0 b=1, cin=1, sum=0, carry=1
At time 4: a=1 b=0, cin=0, sum=1, carry=0
At time 5: a=1 b=0, cin=1, sum=0, carry=1
At time 6: a=1 b=1, cin=0, sum=0, carry=1
At time 7: a=1 b=1, cin=1, sum=1, carry=1

```